




LITAR REKTIFIKASI


RECTIFICATION CIRCUIT

■ Kapasitor Meratakan Arus dalam Litar Rektifikasi Separuh Gelombang

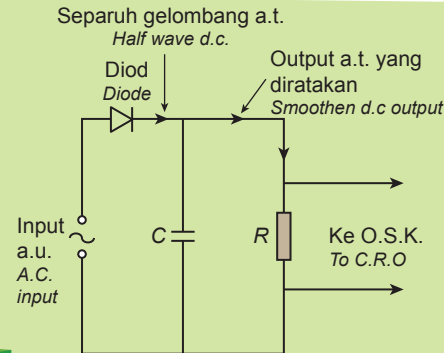Capacitor to Smoothen the Current in a Half-Wave Rectification Circuit





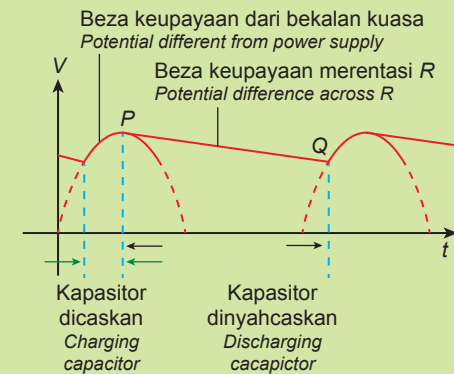Kapasitor harus disambung secara selari dengan perintang.
Capacitor must be connected parallel to the resistor.



■ Kapasitor Meratakan Arus dalam Litar Rektifikasi Penuh Gelombang

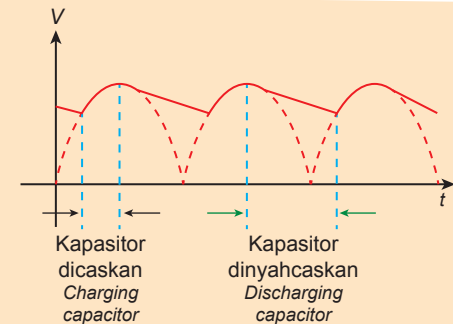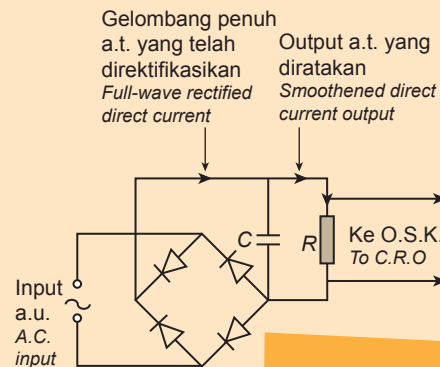Capacitor to Smoothen the Current in a Full-Wave Rectification Circuit



Arus yang dinyhaskan daripada kapasitor membantu dalam meratakan beza keupayaan output merentasi suatu perintang.
Current from the discharging capacitor helps in smoothing the output potential difference across the resistor.